

Government Engineering College, Dahod (018)
Computer Engineering Department (07)
Semester: 2nd
Tutorial List
Basic Electronics (2110016)

TUTORIAL-1

- Q.1 Explain Current and Voltage Sources.
- Q.2 Define the following terms :
1. Cycle
 2. Time Period
 3. Frequency
 4. Amplitude
 5. Average Value
 6. RMS Value
 7. Time Constant
- Q.3 Write about the KIRCHOFF'S LAW with the help of diagram.
- Q.4 Write a brief description about wheatrtone Bridge.
- Q.5 Explain : Lumped circuit Elements.